# Q1. BCD TIMECOUNT

## **VERILOG CODE:-**


```
input clock, reset,
    output reg [3:0]dout
    );
 initial dout = 0;
always @ (posedge (clock))
  begin
\Diamond
       if (reset)
          dout <= 0;
⊜
       else if (dout <= 9)
         dout <= dout + 1;
else if (dout == 9)
dout <= 0;
   end
endmodule
```

## **TEST BENCH:-**

```
module bcdcounter_testbench();
reg clock, reset;
wire [3:0] dout;

bcd_counter dut(clock, reset, dout);
initial begin
clock=0;
forever #5 clock=~clock;
end
initial begin
reset=1;
#20;
reset=0;
end
endmodule
```

# RTL SCHEMATIC:-

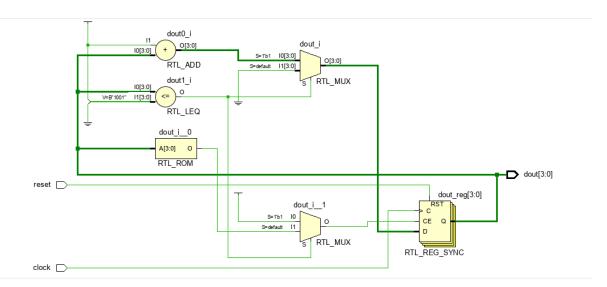

# **SYNTHESIS REPORT:-**

-	t BlackBoxes			
	ackBox name			
-+		-+	+	
epor	t Cell Usage	e:		
	+			
	Cell  Cou			
	+			
1	BUFG	11		
	LUT3			
	LUT4			
	FDRE			
	IBUF			
6	OBUF			
	+	+		
-	t Instance <i>I</i> +			
	Instance			
	+	-+	-+	+
1	top	1	1	161

## POWER REPORT:-

### **♦ Summary**

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 2.855 W
Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 30.4°C

Thermal Margin: 54.6°C (28.8 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

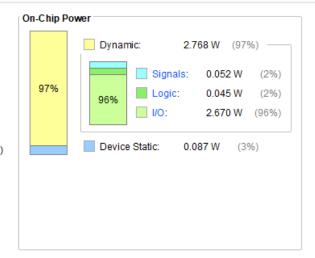

# Q2.3-1 MUX

## **VERILOG CODE:-**

```
module mux_2_1(
   input sel,
   input i0, i1,
   output y);

assign y = sel ? il : i0;
endmodule

module mux_3_1(
   input sel0, sel1,
   input i0,i1,i2,i3,
   output reg y);

wire y0, y1;

mux_2_1 ml(sel1, i0, i1, y0);
   mux_2_1 m2(sel0, y0, i2, y);
endmodule
```

## **TESTBENCH:-**


```
module tb;
  reg sel0, sel1;
  reg i0,i1,i2,i3;
  wire y;

mux_3_1 mux(sel0, sel1, i0, i1, i2, i3, y);

initial begin
  $monitor("sel0=%b, sel1=%b -> i3 = %0b, i2 = %0b ,i1 = %0b, i0 = %0b -> y = %0b", sel0,sel1,i3,i2,i1,i0, y);
  {i3,i2,i1,i0} = 4'h5;

repeat(%) begin
  {sel0, sel1} = $random;
  #5;
  end
  end
endmodule
```


## RTL SCHEMATIC:-

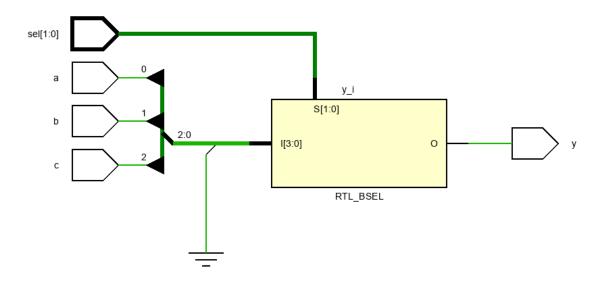

## **SYNTHESIS REPORT:-**

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
     |Cell |Count |
    |LUT5 |
11
12
     |IBUF |
              51
    |OBUF | 1|
13
Report Instance Areas:
+----+
|1 |top | 7|
Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25 . Memory (MB): peak = 1014.996 ; gain = 0.000
```

## POWER REPORT:-

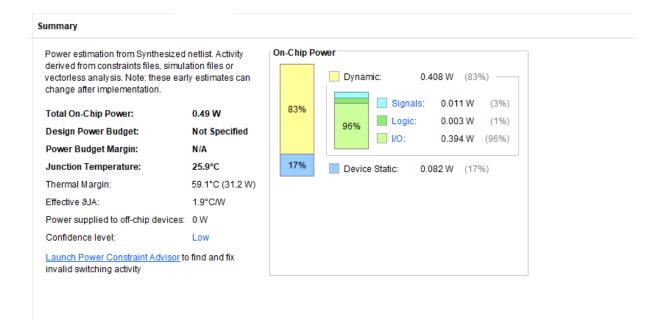

# Q3. BCD TO SEVEN SEGMENT DISPLAY


**VERILOG CODE:-**

```
module segment7(
      bcd.
      seg
       //Declare inputs, outputs and internal variables.
      input [3:0] bcd;
      output [6:0] seg;
      reg [6:0] seg;
 //always block for converting bcd digit into 7 segment format
     always @(bcd)
     begin
         case (bcd) //case statement
             0 : seg = 7'b00000001;
             1 : seg = 7'b1001111;
             2 : seg = 7'b0010010;
             3 : seg = 7'b0000110;
             4 : seg = 7'b1001100;
             5 : seg = 7'b0100100;
             6 : seg = 7'b0100000;
             7 : seg = 7'b0001111;
             8 : seg = 7'b0000000;
             9 : seg = 7'b0000100;
              //switch off 7 segment character when the bcd digit is not a decimal number.
             default : seg = 7'bllllllll;
         endcase
     end
endmodule
```


## **TESTBENCH:-**

```
module tb_segment7;
    reg [3:0] bcd;
   wire [6:0] seg;
    integer i;
    // Instantiate the Unit Under Test (UUT)
    segment7 uut (
        .bcd(bcd),
        .seg(seg)
    );
//Apply inputs
    initial begin
        for(i = 0; i < 16; i = i+1) //run loop for 0 to 15.
        begin
            bcd = i;
            #10; //wait for 10 ns
        end
    end
endmodule
```

# RTL SCHEMATIC:-

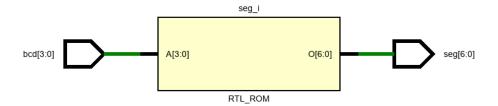

## **SYNTHESIS REPORT:-**

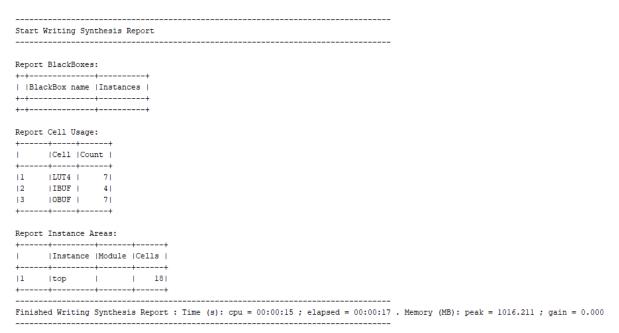

## POWER REPORT:-

#### **Summary**

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.767 W
Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 30.2°C

Thermal Margin: 54.8°C (28.9 W)
Effective \$JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low

<u>Launch Power Constraint Advisor</u> to find and fix

invalid switching activity

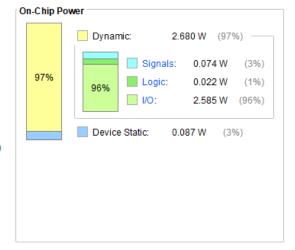


```
module DFFusingMUX(input d1, d0, sel, clk, rst, output reg q);
reg d;
always @ (*)
   begin
       case(sel)
           0 : d = d0;
           1 : d = d1;
       endcase
    end
always @(posedge clk)
    begin
            q \ll 0;
        else
            q \le d;
     end
endmodule
```

# **TESTBENCH:-**

```
module tb;
reg d1,d0;
reg clk;
reg rst;
wire q;
d_latch d3(q,d1,d0,clk,rst);
initial
  begin
    clk = 1'b0;
    forever #20 clk = ~clk;
  end
initial
  begin
    rst = 1'b1;
   #40;
rst = 1'b0;
    #40;
    d0 = 1'b0;
    d1= 1'b0;
    #40
    d0 = 1'b1;
    d1 = 1'b0;
    #40;
    $finish;
  end
endmodule
```

## RTL SCHEMATIC:-

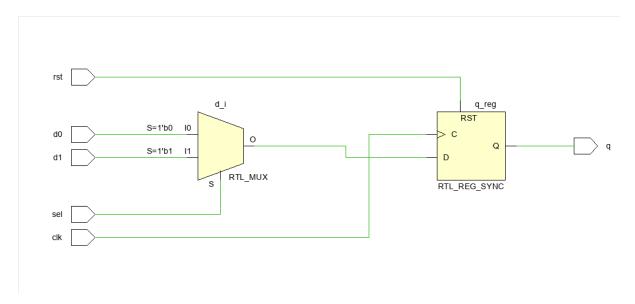

## **SYNTHESIS REPORT:-**

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
      |Cell |Count |
11
13
       |FDRE |
14
      |IBUF |
15
      IOBUF I
                 11
      |Instance |Module |Cells |
11
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:20 . Memory (MB): peak = 1019.727 ; gain = 0.000
```

## POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.


0.457 W Total On-Chip Power: Design Power Budget: Not Specified Power Budget Margin: N/A Junction Temperature: 25.9°C

59.1°C (31.2 W) Thermal Margin: 1.9°C/W Effective 9JA: Power supplied to off-chip devices: 0 W

Confidence level:

Launch Power Constraint Advisor to find and fix

invalid switching activity

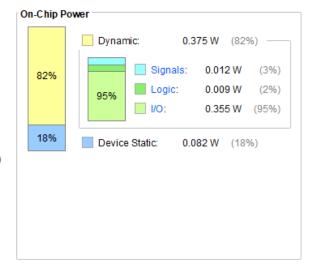


# Q5.8-BIT BARREL SHIFTER

```
module barrel_shifter_8bit (in, ctrl, out);
   input [7:0] in;
   input [2:0] ctrl;
   output [7:01 out:
   wire [7:0] x,y;
  //4bit shift right
 mux2X1 ins_17 (.in0(in[7]),.in1(1'b0),.sel(ctrl[2]),.out(x[7]));
 mux2X1 ins_16 (.in0(in[6]),.in1(1'b0),.sel(ctrl[2]),.out(x[6]));
 mux2X1 ins_15 (.in0(in[5]),.in1(1'b0),.sel(ctrl[2]),.out(x[5]));
 mux2X1 ins_14 (.in0(in[4]),.in1(1'b0),.sel(ctr1[2]),.out(x[4]));
 mux2X1 ins 13 (.in0(in[3]),.inl(in[7]),.sel(ctrl[2]),.out(x[3]));
 mux2X1 ins_12 (.in0(in[2]),.inl(in[6]),.sel(ctrl[2]),.out(x[2]));
 mux2X1 ins_11 (.in0(in[1]),.inl(in[5]),.sel(ctrl[2]),.out(x[1]));
 mux2X1 ins_10 (.in0(in[0]),.inl(in[4]),.sel(ctrl[2]),.out(x[0]));
 //2 bit shift right
 mux2X1 ins_27 (.in0(x[7]),.in1(1'b0),.sel(ctrl[1]),.out(y[7]));
 mux2X1 ins_26 (.in0(x[6]),.in1(1'b0),.sel(ctrl[1]),.out(y[6]));
 mux2X1 ins_25 (.in0(x[5]),.inl(x[7]),.sel(ctrl[1]),.out(y[5]));
 \label{eq:mux2X1} \mbox{ ins\_24 } \mbox{ (.in0} \mbox{ (x[4]),.inl} \mbox{ (x[6]),.sel} \mbox{ (ctrl[1]),.out} \mbox{ (y[4]));}
 mux2X1 ins_23 (.in0(x[3]),.inl(x[5]),.sel(ctrl[1]),.out(y[3]));
 mux2X1 ins_22 (.in0(x[2]),.in1(x[4]),.sel(ctrl[1]),.out(y[2]));
 \label{eq:mux2X1} \  \  ins\_21 \  \, (.in0\,(x\,[1])\,,.inl\,(x\,[3])\,,.sel\,(ctrl\,[1])\,,.out\,(y\,[1]))\,;
 \label{eq:mux2X1} \mbox{ ins\_20 } (.\mbox{in0}(x[0]),.\mbox{in1}(x[2]),.\mbox{sel}(\mbox{ctrl}[1]),.\mbox{out}(y[0]));
  //1 bit shift right
 mux2X1 ins_07 (.in0(y[7]),.in1(1'b0),.sel(ctrl[0]),.out(out[7]));
 \label{eq:mux2X1} \  \  ins\_06 \  \, (.in0(y[6]),.in1(y[7]),.sel(ctrl[0]),.out(out[6]));
 mux2X1 ins_05 (.in0(y[5]),.in1(y[6]),.sel(ctrl[0]),.out(out[5]));
 \verb|mux2X1 ins_04 (.in0(y[4]),.in1(y[5]),.sel(ctr1[0]),.out(out[4]));\\
  mux2X1 ins_03 (.in0(y[3]),.in1(y[4]),.sel(ctr1[0]),.out(out[3]));
 mux2X1 ins 02 (.in0(y[2]),.in1(y[3]),.sel(ctrl[0]),.out(out[2]));
  //2 bit shift right
  mux2X1 ins_27 (.in0(x[7]),.in1(1'b0),.sel(ctrl[1]),.out(y[7]));
  mux2X1 ins 26 (.in0(x[6]),.inl(1'b0),.sel(ctrl[1]),.out(y[6]));
  mux2X1 ins_25 (.in0(x[5]),.in1(x[7]),.sel(ctrl[1]),.out(y[5]));
  mux2X1 ins 24 (.in0(x[4]),.in1(x[6]),.sel(ctrl[1]),.out(y[4]));
  mux2X1 ins_23 (.in0(x[3]),.inl(x[5]),.sel(ctrl[1]),.out(y[3]));
  mux2X1 ins_22 (.in0(x[2]),.inl(x[4]),.sel(ctrl[1]),.out(y[2]));
  mux2X1 ins_21 (.in0(x[1]),.in1(x[3]),.sel(ctrl[1]),.out(y[1]));
  mux2X1 ins_20 (.in0(x[0]),.inl(x[2]),.sel(ctrl[1]),.out(y[0]));
  //1 bit shift right
  mux2X1 ins_07 (.in0(y[7]),.in1(1'b0),.sel(ctrl[0]),.out(out[7]));
  mux2X1 ins_06 (.in0(y[6]),.inl(y[7]),.sel(ctrl[0]),.out(out[6]));
  mux2X1 ins_05 (.in0(y[5]),.inl(y[6]),.sel(ctrl[0]),.out(out[5]));
  mux2X1 ins_04 (.in0(y[4]),.inl(y[5]),.sel(ctrl[0]),.out(out[4]));
  mux2X1
           ins_03 (.in0(y[3]),.in1(y[4]),.sel(ctrl[0]),.out(out[3]));
  mux2X1 ins_02 (.in0(y[2]),.in1(y[3]),.sel(ctrl[0]),.out(out[2]));
  mux2X1
           ins_01 (.in0(y[1]),.in1(y[2]),.sel(ctrl[0]),.out(out[1]));
  mux2X1 ins_00 (.in0(y[0]),.in1(y[1]),.sel(ctrl[0]),.out(out[0]));
endmodule
  //2X1 Mux
module mux2X1( in0,in1,sel,out);
  input in0, in1;
  input sel;
  output out;
  assign out=(sel)?inl:in0;
endmodule
```

## **TESTBENCH:-**

```
module barrel_shifter_8bit_tb;
   reg [7:0] in;
   reg [2:0] ctrl;
   wire [7:0] out;
 barrel_shifter_8bit uut(.in(in), .ctrl(ctrl), .out(out));
initial
begin
     $display($time, " << Starting the Simulation >>");
         in= 8'd0; ctrl=3'd0; //no shift
     #10 in=8'd128; ctrl= 3'd4; //shift 4 bit
     #10 in=8'd128; ctrl= 3'd2; //shift 2 bit
     #10 in=8'd128; ctrl= 3'd1; //shift by 1 bit
     #10 in=8'd255; ctrl= 3'd7; //shift by 7bit
   end
     initial begin
       $monitor("Input=%d, Control=%d, Output=%d",in,ctrl,out);
     end
endmodule
```

## RTL SCHEMATIC:-

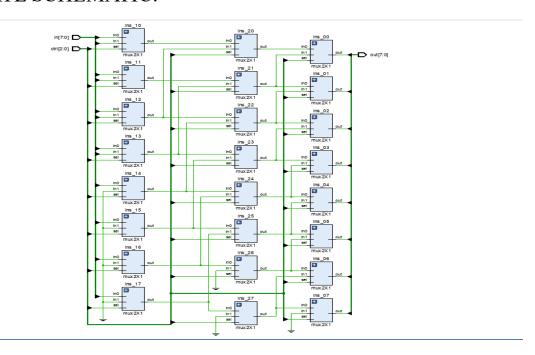

### SYNTHESIS REPORT:-

## POWER REPORT:-

#### **Summary**

On-Chip Power Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can Dynamic: 2.817 W (97%) change after implementation. Signals: 0.132 W (5%) Total On-Chip Power: 2.904 W 97% Logic: 0.045 W (2%)93% Design Power Budget: Not Specified 2.639 W (93%) Power Budget Margin: N/A Junction Temperature: 30.5°C Device Static: 0.087 W (3%) Thermal Margin: 54.5°C (28.8 W) Effective 9JA: 1.9°C/W Power supplied to off-chip devices: 0 W Confidence level: Launch Power Constraint Advisor to find and fix invalid switching activity

## Q6. 1-BIT COMPARATOR USING 4X1 MUX

```
module comp_lbit(out, a, b, c, d, s0, s1);


output out;
input a, b, c, d, s0, s1;
wire sobar, slbar, T1, T2, T3, T4;

not (s0bar, s0), (slbar, s1);
and (T1, a, s0bar, slbar), (T2, b, s0bar, s1),(T3, c, s0, slbar), (T4, a, s0, s1);
or(out, T1, T2, T3, T4);
endmodule
```

#### **TESTBENCH:-**

```
) module tb;
 wire out;
  reg a:
  reg b;
  reg c;
  reg d;
  reg s0, s1;
 m41 name(.out(out), .a(a), .b(b), .c(c), .d(d), .s0(s0), .s1(s1));
) initial
) begin
  a=1'b0; b=1'b0; c=1'b0;
  s0=1'b0; s1=1'b0;
  #500 $finish;
) end
 always #40 a=~a;
 always #20 b=~b;
 always #10 c=~c;
 always #80 s0=~s0;
 always #160 sl=~sl;
) always@(a or b or c or s0 or s1)
) $monitor("At time = %t, Output = %d", $time, out);
) endmodule
```

### RTL SCHEMATIC:-

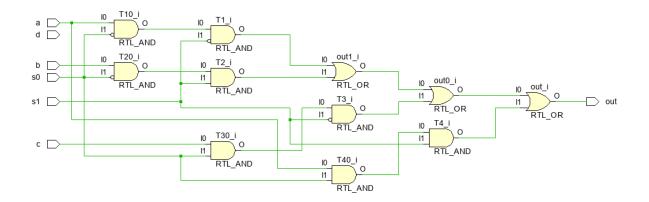

### **SYNTHESIS REPORT:-**

## POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.531 W

Design Power Budget: Not Specified

Power Budget Margin: N/A


Junction Temperature: 26.0°C

Thermal Margin: 59.0°C (31.1 W)

Effective 9JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

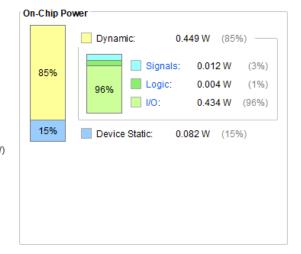


Q7.LOGICAL, ALGEBRAIC, AND ROTATE SHIFT OPERATIONS

```
module shift_rotate (a, opcode, result);
 input [7:0] a;
 input [2:0] opcode;
 output [7:0] result;
 wire [7:0] a;
 wire [2:0] opcode;
) reg [7:0] result;
 parameter sra_op = 3'b000,
 srl op = 3'b001,
 sla_op = 3'b010,
 sll op = 3'b011,
 ror_op = 3'b100,
 rol_op = 3'b101;
always @ (a or opcode)
begin
case (opcode)
) sra_op : result = {a[7], a[7], a[6], a[5],
) a[4], a[3], a[2], a[1]};
 srl op : result = a >> 1;
) sla_op : result = {a[6], a[5], a[4], a[3],
) a[2], a[1], a[0], 1'b0};
  sll_op : result = a << 1;
ror_op : result = {a[0], a[7], a[6], a[5],
) a[4], a[3], a[2], a[1]};
rol_op : result = {a[6], a[5], a[4], a[3],
) a[2], a[1], a[0], a[7]};
 default : result = 0;
) endcase
) end
) endmodule
```

```
module shift_rotate_tb;
```

```
reg [7:0] a;
     reg [2:0] opcode;
     wire [7:0] result;
     integer i;
     shift_rotate uut (
         .a(a),
         .opcode (opcode),
         .result(result)
     );
     initial begin
     a=8'b10110101;
     opcode = 000;
     end
     initial
     begin
     for(i=0;i<6;i=i+1)
     begin
     opcode=i;
     #10;
     end
     end
     initial
     $monitor(" A=%b | Opcode=%b | Result =%b ",a,opcode,result);
endmodule
```

## RTL SCHEMATIC:-

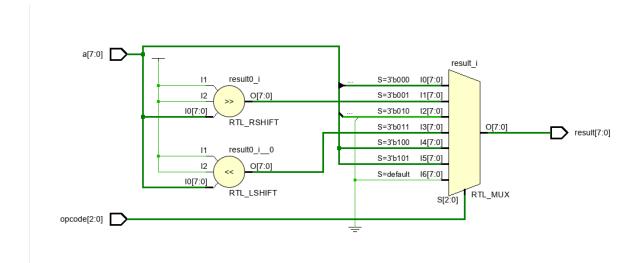

## **SYNTHESIS REPORT:-**

Start Writing Synthesis Report

Report BlackBoxes:

| |BlackBox name |Instances | +-+----+

Report Cell Usage:

Report Instance Areas:

Finished Writing Synthesis Report : Time (s): cpu = 00:00:23 ; elapsed = 00:00:33 . Memory (MB): peak = 1017.926 ; gain = 0.000

### POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 3.055 W

Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 30.8°C

Thermal Margin: 54.2°C (28.6 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix


invalid switching activity

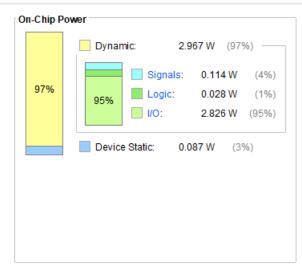

```
module alu (a, b, opcode, rslt);
input [3:0] a, b;
input [2:0] opcode;
output [7:0] rslt;
reg [7:0] rslt;
parameter add_op = 3'b000,
sub_op = 3'b001,
mul_op = 3'b010,
and op = 3'b011,
or_op = 3'b100,
not_op = 3'b101,
xor_op = 3'b110,
xnor_op = 3'blll;
always @ (a or b or opcode)
begin
case (opcode)
add_op: rslt = a + b;
sub_op: rslt = a - b;
mul op: rslt = a * b;
and_op: rslt = a & b; //also ab
or_op: rslt = a | b;
not_op: rslt = ~a; //also ~b
xor_op: rslt = a ^ b;
xnor_op: rslt = ~(a ^ b);
endcase
end
endmodule
```

```
`timescale lns / lps
module alu tb;
     reg [3:0] a;
     reg [3:0] b;
     reg [2:0] opcode;
     wire [7:0] rslt;
     alu uut (.a(a), .b(b), .opcode(opcode), .rslt(rslt));
     initial
     begin
 #0 a = 4'b0001; b = 4'b0010; opcode = 3'b000;
 #10 a = 4'b0110; b = 4'b0110; opcode = 3'b000;
 #10 a = 4'b1100; b = 4'b0011; opcode = 3'b001;
 #10 a = 4'b1101; b = 4'b1010; opcode = 3'b001;
 #10 a = 4'b1100; b = 4'b0111; opcode = 3'b010;
 #10 a = 4'b1111; b = 4'b0011; opcode = 3'b010;
 #10 a = 4'b1100; b = 4'b0111; opcode = 3'b011;
 #10 a = 4'b1101; b = 4'b1011; opcode = 3'b011;
 #10 a = 4'b0101; b = 4'b1011; opcode = 3'b100;
 #10 a = 4'b1001; b = 4'b1010; opcode = 3'b100;
 #10 a = 4'b1001; opcode = 3'b101;
 #10 a = 4'b0011; opcode = 3'b101;
 #10 a = 4'b0111; b = 4'b1011; opcode = 3'b110;
 #10 a = 4'b1010; b = 4'b0101; opcode = 3'b110;
 #10 a = 4'b0110; b = 4'b0110; opcode = 3'b111;
 #10 a = 4'b0011; b = 4'b1110; opcode = 3'b111;
end
 initial
 begin
 $monitor(" A=%b | B=%b | Opcode = %b | Result=%b",a,b,opcode,rslt);
 #300 $finish;
endmodule
```


#### RTL SCHEMATIC:-

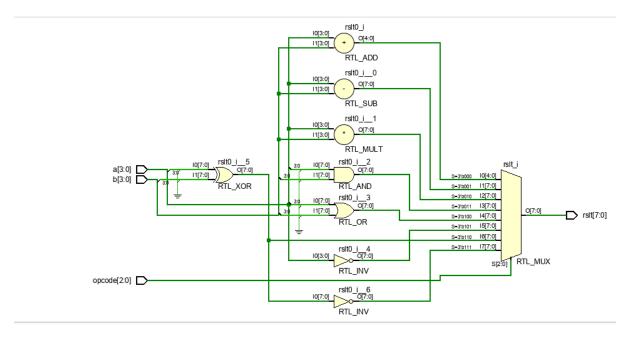

### **SYNTHESIS REPORT:-**

Start Writing Synthesis Report | |BlackBox name |Instances | Report Cell Usage: |CARRY4 | |LUT2 | |LUT4 |LUT5 |LUT6 | 19| |MUXF7 | 3| | IBUF 111 |OBUF | 8 | Report Instance Areas: |Instance |Module |Cells | Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:21 . Memory (MB): peak = 1016.625 ; gain = 0.000

### POWER REPORT:-

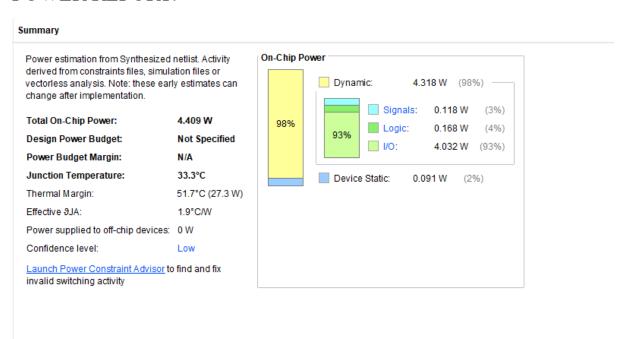


## Q9. 4-BIT ASYNCHRONOUS DOWN COUNTER

```
module dff(q,qbar,clk,rst,d);
   output reg q;
    output qbar;
    input clk, rst;
    input d;
    assign qbar = ~q;
    always @(posedge clk, posedge rst)
    begin
        if (rst)
           q \ll 0;
        else
           q <= d;
    end
endmodule
module async_counter(count,countbar,clk,rst);
  input clk, rst;
 output [3:0] count, countbar;
    dff dffl(count[0],countbar[0],clk
                                        ,rst,countbar[0]);
 dff dff2(count[1],countbar[1],count[0],rst,countbar[1]);
 dff dff3(count[2],countbar[2],count[1],rst,countbar[2]);
  dff dff4(count[3],countbar[3],count[2],rst,countbar[3]);
```

endmodule

```
module async_counter_tb;
      // Inputs
     reg clk;
     reg rst;
      // Outputs
     wire [3:0] count;
     wire [3:0] countbar;
      // Instantiate the Unit Under Test (UUT)
     async_counter uut (
         .count (count),
         .countbar(countbar),
         .clk(clk),
         .rst(rst)
     );
) initial
   begin
     clk = 0;
     rst = 1;
     #23;// Just give enough time to reset the design
     rst = 0;
     #200;
     $finish;
   end
    always #5 clk = ~clk;
endmodule
```

## RTL SCHEMATIC:-

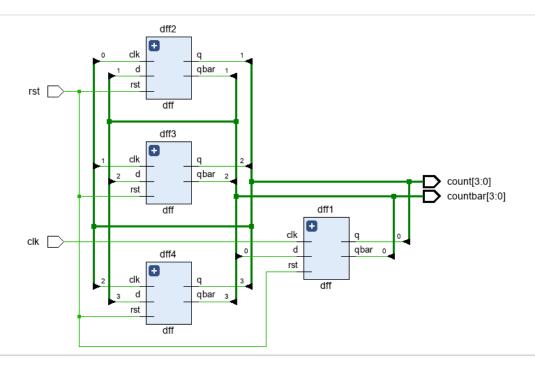

## **SYNTHESIS REPORT:-**


```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
      |Cell |Count |
      IBUFG I
11
12
      |LUT1 |
      I FDCE
      |IBUF |
      |OBUF |
Report Instance Areas:
      |Instance |Module |Cells |
      | dffl
12
|3
|4
       | dff2 |dff_0 |
      | dff3 |dff 1 |
Finished Writing Synthesis Report : Time (s): cpu = 00:00:27 ; elapsed = 00:00:37 . Memory (MB): peak = 1017.906 ; gain = 0.000
```

### POWER REPORT:-
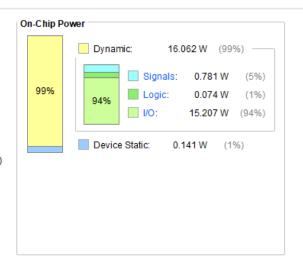
#### Summary

vectorless analysis. Note: these early estimates can change after implementation. 16.203 W Total On-Chip Power: Design Power Budget: Not Specified Power Budget Margin: N/A Junction Temperature: 55.5°C Thermal Margin: 29.5°C (15.5 W) Effective 9JA: 1.9°C/W Power supplied to off-chip devices: 0 W Confidence level: Launch Power Constraint Advisor to find and fix invalid switching activity

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or




```
`timescale lns / lps
module modN_counter
   # (parameter N = 10,
     parameter WIDTH = 4)
   ( input clk,
    input reset,
    input upordown,
    output reg[WIDTH-1:0] count);
   always @ (posedge clk )
   begin
    if (reset==1)
     count <= 0;
    else
    if(upordown==1)
                     //Up Mode is selected
          if (count == N-1)
      count <= 0;
            else
        count<=count+1; //increment counter
                      //Down Mode is selected
    else
      if(count==0)
    count<=N-1;
       else
      count<=count-1; //Decrement the counter
   end
```

endmodule

**TESTBENCH:-**

```
`timescale lns / lps
module modN_updown_tb;
      reg clk;
      reg reset;
      reg upordown;
      wire [3:0] count;
      modN counter uut (
          .clk(clk),
          .reset (reset),
          .upordown (upordown),
          .count (count)
      );
9
      initial begin
          clk = 0;
          reset = 1;
           #50 reset =0; upordown = 0;
          #200;
          upordown = 1;
        #200;
          reset = 1;
          upordown = 0;
          #100;
          reset = 0;
) end
  always #10 clk=~clk;
) initial
) begin
  $monitor("UporDown=%b | Count=%b",upordown,count);
  #1000 $finish;
end)
endmodule
```

## RTL SCHEMATIC:-

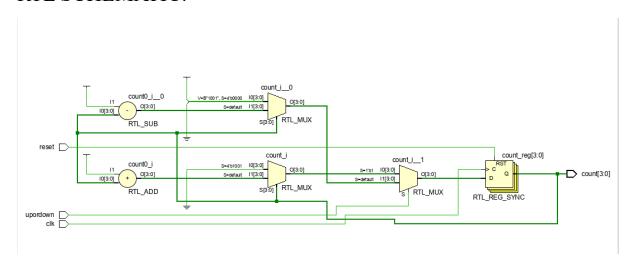

## SYNTHESIS REPORT:-

## POWER REPORT:-

#### Summary

On-Chip Power Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can Dynamic: 3.716 W (98%) change after implementation. Signals: 0.140 W (4%) Total On-Chip Power: 3.805 W 98% Logic: 0.053 W (1%) 95% Design Power Budget: Not Specified 3.522 W (95%) Power Budget Margin: N/A 32.2°C Junction Temperature: Device Static: 0.089 W (2%) 52.8°C (27.9 W) Thermal Margin: Effective 9JA: Power supplied to off-chip devices: 0 W Confidence level: Launch Power Constraint Advisor to find and fix invalid switching activity


# Q11. UNIVERSAL BINARY COUNTER

```
`timescale lns / lps
module univ_bin_counter
 # (parameter N=8)
  (
 input wire clk, reset,
 input wire syn_clr , load, en, up,
 input wire [N-1:0] d,
 output wire max, min,
 output wire [N-1:0] q
 );
 reg [N-1:0] r_reg, r_next;
always @(posedge clk, posedge reset)
if (reset)
r_reg <= 0; //
 else
r_reg <= r_next;
always @(*)
if (syn clr)
 r_next = 0;
else if (load)
 r_next = d;
else if (en & up)
 r_next = r_reg + 1;
else if (en & ~up)
 r next = r reg - 1;
 else
r_next = r_reg;
 assign q = r_reg;
 assign max = (r_reg==2**N-1) ? 1'b1 : 1'b0;
 assign min = (r_reg==0) ? 1'b1 : 1'b0;
endmodule
```

#### **TESTBENCH:-**

```
'timescale lns / lps
module univ bin counter tb;
       reg clk;
       reg reset;
       reg load;
       reg en;
       reg up;
       reg [7:0] d;
       wire max;
       wire [7:0] q;
   univ\_bin\_counter\ uut\ (.clk(clk),\ .reset(reset),\ .syn\_clr(syn\_clr),\ .load(load),\ .en(en),\ .up(up),\ .d(d),\ .max(max),\ .min(min),\ .q(q)); 
       initial begin
           clk = 0;
           reset = 0;
            syn_clr = 0;
            load = 0;
           en = 0;
up = 0;
            d = 0;
            #10 reset =1; syn clr=1; load=1; en=1;up=1; d=1;
            #10 reset =0; syn_clr=0; load=1; en=1;up=1; d=1;
#10 reset =0; syn_clr=0; load=0; en=1;up=1; d=1;
            #400 reset =0;syn_clr=0 ; load=0; en=1;up=0; d=1;
       end
       initial
       $monitor(" Reset=%b | Sync clr=%b | Load=%b| En=%b | Up=%b| D=%b | Q=%b", reset, syn_clr, load, en, up, d, q);
       #1000 $finish;
       end
endmodule
```

#### RTL SCHEMATIC:-

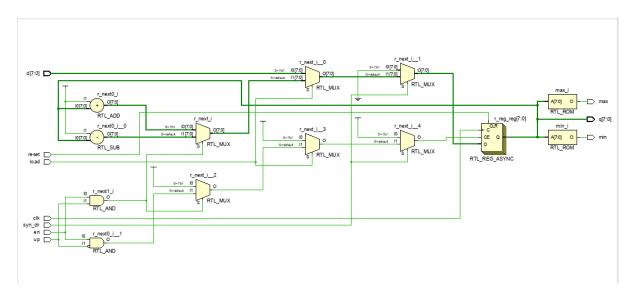

# SYNTHESIS REPORT:-

•	BlackBox			
Blac	kBox nam	ne   ]	instand	ces
-	Cell Usa -+	_	+	
I	Cell			
+   1	BUFG	1		
	CARRY4	Ĺ	2	
3	LUT1	L	11	
4	LUT2	1	61	
15	LUT3	1	2	
16	LUT4	1	10	
	LUT5			
			81	
			14	
10		I		
	-+	+	+	
Report	Instance	Are	as:	
	+			
	Instanc			
	+			
	top -+			

# POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 3.709 W
Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 32.0°C

Thermal Margin: 53.0°C (28.0 W)


Effective 9JA: 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

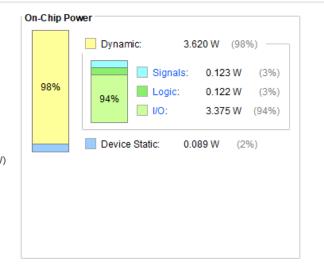


# Q12. UNIVERSAL SHIFT REGISTER

```
`timescale lns / lps
module universal_shiftreg(DATAOUT, clock, reset, MODE, DATAIN);
    output reg [3:0] DATAOUT;
    input clock, reset;
   input [1:0] MODE;
   input [3:0] DATAIN;
    always @(posedge clock)
   begin
     if (reset)
       DATAOUT <= 0;
       begin
         case (MODE)
                                          // locked mode, do nothing
           2'b00 : DATAOUT <= DATAOUT;
            2'b01 : DATAOUT <= {DATAIN[0], DATAIN[3:1]};//DATAOUT >> 1;
           2'bl0 : DATAOUT <= {DATAIN[2:0], DATAIN[3]};//DATAOUT << 1;
           2'bl1 : DATAOUT <= DATAIN;
                                          // parallel in parallel out
          endcase
        end
endmodule
```


#### **TESTBENCH:-**

```
`timescale lns / lps
 module univ_bin_counter_tb;
       reg clk;
       red reset:
       reg syn_clr;
       reg load;
       reg en;
       reg up;
       reg [7:0] d;
       wire max;
       wire [7:0] q;
       univ bin_counter uut (.clk(clk), .reset(reset), .syn_clr(syn_clr), .load(load), .en(en), .up(up), .d(d), .max(max), .min(min), .q(q));
           clk = 0:
           reset = 0;
            syn_clr = 0;
           load = 0;
           en = 0;
            up = 0;
           d = 0:
           #10 reset =1; syn_clr=1; load=1; en=1;up=1; d=1;
           #10 reset =0; syn_clr=0; load=1; en=1;up=1; d=1;
#10 reset =0; syn_clr=0; load=0; en=1;up=1; d=1;
#400 reset =0;syn_clr=0; load=0; en=1;up=0; d=1;
       always #5 clk=~clk;
       begin
       $monitor(" Reset=%b | Sync_clr=%b | Load=%b| En=%b | Up=%b| D=%b | Q=%b",reset,syn_clr,load,en,up,d,q);
endmodule
```

## RTL SCHEMATIC:-

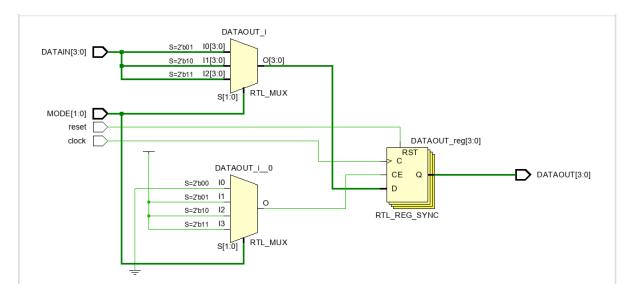

## SYNTHESIS REPORT:-

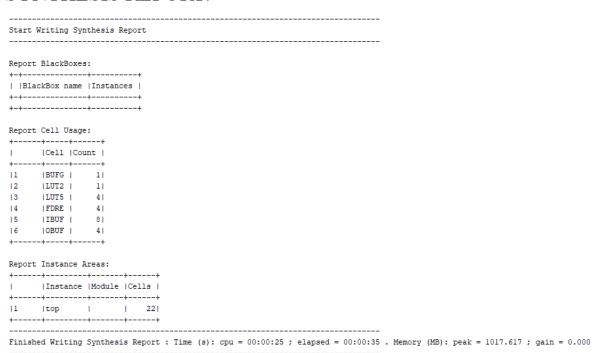

### POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:

Design Power Budget:

Not Specified

N/A

Junction Temperature:

Thermal Margin:

Effective 9JA:


Power supplied to off-chip devices:

Confidence level:

Low

Launch Power Constraint Advisor to find and fix

invalid switching activity

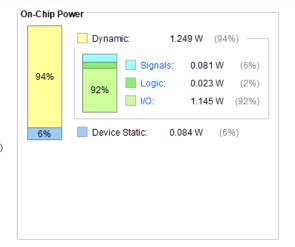

Q13. CN( CHANGE-NO CHANGE FLIPFLOP) USING 2:1 MUX


## **VERILOG CODE:-**

```
module mux2X1(a,b,s,y);
input a,b,s;
output reg y;
always @(a or b or s)
begin
case(s)
0: y=a;
1:y=b;
default: y=1'b0;
endcase
end
endmodule
module d_ff(d,clk,reset,q);
input d,clk,reset;
output reg q;
always @(posedge clk)
begin
if(reset)
q=0;
else
q=d;
end
endmodule
module cn_flipflop(c,n,clk,q,qbar);
input c,n,clk;
output q,qbar;
wire cn,n_bar,d_wire;
mux2X1 mux1(1'b0,c,n,cn);
mux2X1 mux2(1'b1,1'b0,n,n_bar);
mux2X1 mux3(cn,n_bar,q,d_wire);
{\tt d\_ff\ dffl(\ .d(d\_wire),.clk(clk),.reset(),.q(q));}
assign qbar=~q;
endmodule
```

#### 21EL034

```
`timescale lns / lps
module cn_flipflop_tb;
      reg c;
      reg n;
      reg clk;
      wire q,qbar;
      \verb|cn_flipflop uut (.c(c),.n(n),.clk(clk),.q(q),.qbar(qbar))|;
      initial begin
           c = 0;
n = 0;
           clk = 0;
           #10 c=0;n=1;
           #10 c=1;n=0;
           #10 c=1;n=1;
      always #5 clk=~clk;
      initial
      \label{local_property}  \texttt{begin \$monitor("C=\$b | N=\$b | Q=\$b | Qbar=\$b",c,n,q,qbar);} 
      #100 $finish;
) endmodule
```

## RTL SCHEMATIC:-

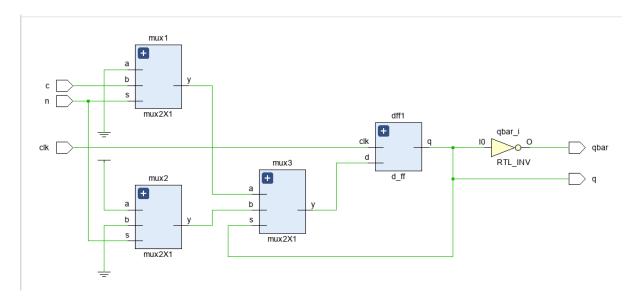

## SYNTHESIS REPORT:-

#### 21EL034

Start Writing Synthesis Report Report BlackBoxes: | |BlackBox name |Instances | Report Cell Usage: |Cell |Count | IBUFG I 11 ILUT1 | 12 11 |LUT3 | 13 |4 |FDRE | |IBUF | |OBUF | Report Instance Areas: |Instance |Module |Cells | 11 |top | dffl |d\_ff

Finished Writing Synthesis Report : Time (s): cpu = 00:00:24 ; elapsed = 00:00:34 . Memory (MB): peak = 1014.594 ; gain = 0.000


### POWER REPORT:-

#### **Summary**

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 0.856 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.6°C
Thermal Margin: 58.4°C (30.8 W)
Effective JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
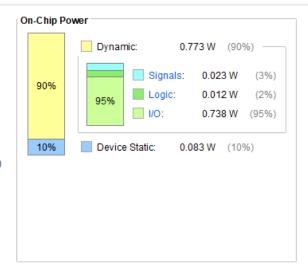
<u>Launch Power Constraint Advisor</u> to find and fix



## **VERILOG CODE:-**

```
`timescale lns / lps
module clk div odd
  #(parameter N=5)
  ( input clk_in,output
                        clk_out);
 reg [3:0] count = 4'b0;
       A1 = 0;
  reg
         B1 = 0;
 reg
       Iff A = 0;
 reg
      Tff_B = 0;
 reg
       clock_out;
 wire
      wTff A;
 wire
 wire wTff B;
 assign wTff_A = Tff_A;
 assign wTff_B = Tff_B;
 assign clk_out = wTff_B ^ wTff_A;
3 always@(posedge clk in)
begin
Э
  if(count == N-1)
9
   begin
    count <= 4'b0000;
   end
É
   else
9
   begin
    count <= count + 1;
É
   end
end
always@(posedge clk_in)
9 begin
if(count == 4'b0000)
   A1 <= 1;
   else
    A1 <= 0;
end
```


#### 21EL034

```
A1 <= 0;
end
always@(posedge clk_in)
begin
if(count == (N+1)/2)
   B1 <= 1;
  else
B1 <= 0;
end
always@(negedge Al)
begin
  Tff A <= ~Tff A;
end
always@(negedge clk_in)
begin
if(B1)
  begin
    Tff_B <= ~Tff_B;
  end
end
endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module clk_div_odd_tb;
      reg clk_in;
      wire clk_out;
  clk_div_odd uut (
          .clk_in(clk_in),
          .clk_out(clk_out)
      );
)
     initial begin
        clk_in=1;
         end
)
      always #10 clk_in= ~clk_in;
)
     initial
      #200 $finish;
) endmodule
```


## RTL SCHEMATIC:-

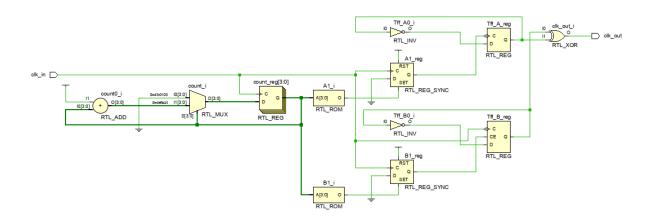

## SYNTHESIS REPORT:-

Start	Writing S	Synthesis	Report
Repor	t BlackBox	tes:	
+-+		+	+
B1	ackBox nar	ne  Instan	nces
+-+		+	+
+-+		+	+
_	t Cell Usa	_	
	++-		
l	Cell  C		
	++-		
1	BUFG	11	
12	LUT1	2	
3	LUT2	3	
4	LUT3	11	
5	LUT4	41	
7	FDRE		
8	IBUF	11	
	OBUF	11	
,	++-	+	
encr	t Instance	Areas:	
_			++
			Cells
+	+		
	top	i	1 211
-	+		

## POWER REPORT:-

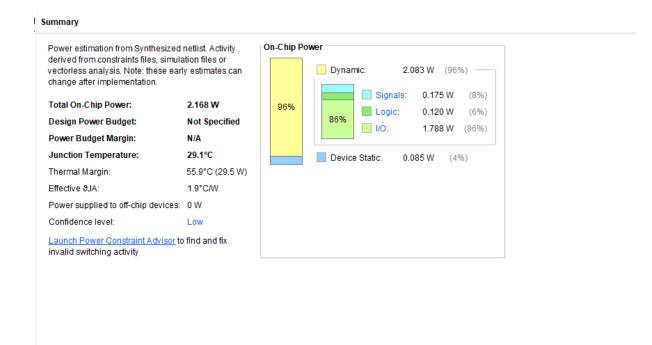

# Q15. GREATEST COMMON DIVISOR USING BEHAVIOURAL MODELLING

## **VERILOG CODE:-**

```
`timescale lns / lps
module gcd_beh #( parameter W = 4)
  input [W-1:0] A, B,
  input clk, rst,
  output reg [W-1:0] GCD
  );
  reg [W-1:0] Ain, Bin;
3 always @(posedge clk or negedge rst)

  begin

  Ain = A; Bin = B;
d while ( Ain != Bin)
9 begin

if ( Ain < Bin )

</pre>
  Bin = Bin-Ain;
  else
Ain = Ain - Bin;
end
  GCD = Ain;
endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module gcd beh tb;
  parameter W=7;
     reg [W-1:0] A;
     reg [W-1:0] B;
     wire [W-1:0] GCD;
     gcd_beh uut (.A(A),.B(B),.GCD(GCD));
     initial begin
         A=90;B=86;
          #10 A=48; B=12;
          #10 A=65;B=4;
          #10 A=48;B=7;
          #10 A=8;B=2;
          #10 A=125;B=6;
          #10 A=85;B=76;
         #10 A=54;B=44;
         #10 A=95;B=32;
          #10 A=109;B=91;
          #10 A=75;B=34;
Ė
    end
9
       initial
Э
          begin
          $monitor("A= %d | B=%d | GCD=%d", A,B,GCD);
         #200 $finish;
         end
endmodule
```


# Q16.SINGLE PORT RAM VERILOG CODE:-

```
module single_port_ram
#(parameter addr_width = 6,
parameter data_width = 8,
parameter depth = 64)
               input [data_width-1:0] data,
                input [addr_width-1:0] addr,
               input we,clk,
               output [data_width-1:0] q
reg [data_width-1:0] ram [depth-1:0];
reg [addr_width-1:0] addr_reg;
always @(posedge clk)
if(we)
     ram[addr] <=data;
     else
        addr_reg <=addr;
assign q= ram[addr_reg];
endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module single_port_ram_tb;
 parameter addr_width = 6;
 parameter data_width = 8;
 parameter depth = 64;
      reg [data_width-1:0] data;
      reg [addr_width:0] addr;
      reg we;
      reg clk;
      wire [data_width-1:0] q;
      single_port_ram \ uut \ (.data(data),.addr(addr), .we(we),.clk(clk),.q(q));
     initial begin
          clk=0;
          forever #5 clk=~clk;
end)
initial begin
 data=8'h01;
  addr=5'd0;
  we=1'b1;
  data=8'h02;
  addr=5'd1;
  #10;
  data=8'h03;
  addr=5'd2;
  #10;
  addr=5'd0;
  we=1'b0;
  #10;
  addr=5'd1;
  #10;
  addr=5'd2;
  #10;
end)
) endmodule
```

## RTL SCHEMATIC:-

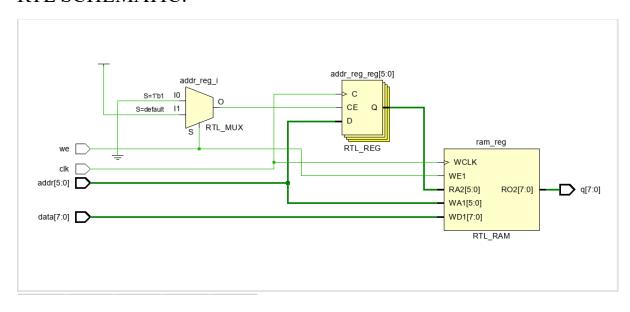

## **SYNTHESIS REPORT:-**

Start Writing Synthesis Report Report BlackBoxes: | |BlackBox name |Instances | Report Cell Usage: |BUFG | 1| |LUT1 | 1| |RAM64M | 2| |RAM64X1D | 2| 11 12 13 | 4 15 FDRE 16 | IBUF OBUF Report Instance Areas: | | | | Instance | Module | Cells | |1 |top | | 36|

Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:18 . Memory (MB): peak = 1017.363 ; gain = 0.000

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 2.194 W

Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 29.1°C

Thermal Margin: 55.9°C (29.5 W)

Effective 3JA: 1.9°C/W
Power supplied to off-chip devices: 0 W

Confidence level: Low

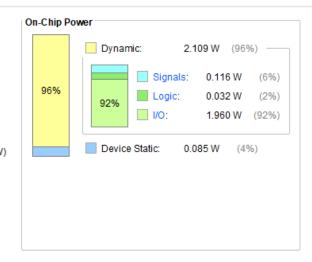Launch Power Constraint Advisor to find and fix



## Q17. DUAL PORT RAM

## **VERILOG CODE:-**


```
module dual_port_ram
       # (parameter data_width=8,
           parameter addr_width=4,
              parameter depth=16
  ( input clk,
          input wr_en,
          input [data_width-1:0] data_in,
          input [addr width-1:0] addr in 0,
          input [addr_width-1:0] addr_in_1,
          input port_en_0,
         input port_en_1,
         output [data_width-1:0] data_out_0,
         output [data_width-1:0] data_out_1
      );
  reg [data_width-1:0] ram[0:depth-1];
always@(posedge clk)
9 begin
Э
      if (port en 0 == 1 && wr en == 1)
         ram[addr_in_0] <= data_in;
end)
  assign data_out_0 = port_en_0 ? ram[addr_in_0] : 'dZ;
  assign data_out_1 = port_en_1 ? ram[addr_in_1] : 'dZ;
endmodule
```

## **TESTBENCH:-**

```
module dual port ram tb;
parameter addr_width = 4;
parameter data_width = 8;
parameter depth = 16;
reg clk;
reg wr_en;
reg [data_width-1:0] data_in;
reg [addr_width-1:0] addr_in_0;
reg [addr_width-1:0] addr_in_1;
reg port_en_0;
wire [data_width-1:0] data_out_0;
wire [data_width-1:0] data_out_1;
dual_port_ram_uut (.clk(clk), .wr_en(wr_en), .data_in(data_in), .addr_in_0(addr_in_0), .addr_in_1(addr_in_1), .port_en_0(port_en_0), .port_en_1(port_en_1),
.data_out_0(data_out_0), .data_out_1(data_out_1);
 always
#5 clk = ~clk;
initial begin clk = 1;
           addr_in_1 = 0;
           port_en_0 = 0;
port_en_1 = 0;
           wr_en = 0;
data_in = 0;
addr_in_0 = 0;
#20;
           port_en_0 = 1;
        wr_en = 1;
for(i=1; i <= 16; i = i + 1) begin
                data in = i:
                 addr_in_0 = i-1;
                #10;
           wr en = 0;
```

```
wr_en = 0;
    port_en_0 = 0;
    port_en_1 = 1;
    for(i=1; i <= 16; i = i + 1) begin
        addr_in_1 = i-1;
        #10;
    end
    port_en_1 = 0;
end
endmodule</pre>
```

## RTL SCHEMATIC:-

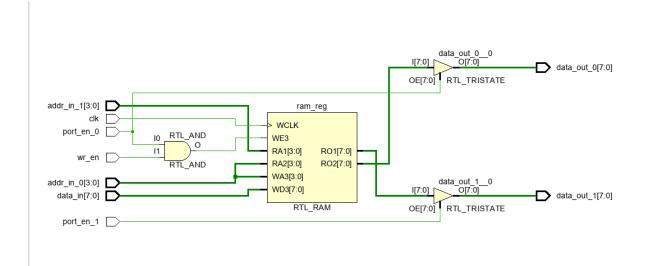

### **SYNTHESIS REPORT:-**

```
Start Writing Synthesis Report
Report BlackBoxes:
| |BlackBox name |Instances |
Report Cell Usage:
     |Cell |Count |
     BUFG
11
      |LUT2
      |RAM16X1D |
15
      IBUF
                    201
     IOBUFT
16
Report Instance Areas:
      |Instance |Module |Cells |
|1 |top | 48|
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:20 . Memory (MB): peak = 1018.852 ; gain = 0.000
```

## POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.233 W


Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature:29.2°CThermal Margin:55.8°C (29.4 W)Effective 9JA:1.9°C/W

Power supplied to off-chip devices: 0 W Confidence level: Low

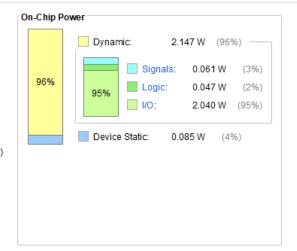Launch Power Constraint Advisor to find and fix



# Q18. CLOCK BUFFER

## **VERILOG CODE:-**

```
`timescale lns / lps
) module clock_buffer(mclk,bclk);
input mclk;
output bclk;
buf bl(bclk,mclk);
endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module clock_buffer_tb();
 reg mclk;
 wire bclk;
 realtime t1, t2, t3, t4, t5, t6;
 parameter T=10;
 clock_buffer dut(mclk,bclk);
) initial
) begin
 mclk=1'b0;
 forever #(T/2) mclk=~mclk;
end
task master;
) begin
 @(posedge mclk) tl=$realtime;
 @(posedge mclk) t2=$realtime;
 t3=t2-t1;
end
endtask
) task bufout;
 @(posedge bclk) t4=$realtime;
 @(posedge bclk) t5=$realtime;
 t6=t5-t4:
end)
endtask
task freq_phase;
 realtime f,p;
) begin
 f=t6-t3;
 p=t4-t1;
 $display("freq_diff=%0t,phase_diff=%0t",f,p);
endtask
initial
begin
fork master;
bufout;
join freq_phase;
end
endmodule
```

## RTL SCHEMATIC:-



## **SYNTHESIS REPORT:-**

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16 . Memory (MB): peak = 1015.395 ; gain = 0.000

## POWER REPORT:-

#### Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.


Total On-Chip Power: 0.333 W Design Power Budget: Not Specified

Power Budget Margin: N/A **Junction Temperature:** 25.6°C

59.4°C (31.3 W) Thermal Margin: 1.9°C/W Effective 9JA: Power supplied to off-chip devices: 0 W

 $\underline{\text{Launch Power Constraint Advisor}} \ \text{to find and fix invalid switching activity}$ 

Confidence level:

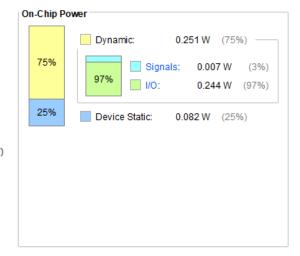

## Q19. SYNCHRONOUS FIFO

## **VERILOG CODE:-**

```
module sync_fifo (input [7:0] data_in, input clk, rst, rd, wr,
output empty, full, output reg [3:0]fifo_cnt,
 output reg [7:0] data_out);
 reg [7:0] fifo_ram [0:7];
reg [2:0] rd ptr, wr ptr;
assign empty= (fifo_cnt==0);
 assign full =(fifo cnt==8);
always @(posedge clk) begin: write

    if (wr && ! full)

fifo_ram [wr_ptr] <= data_in;
else if (wr && rd)
fifo_ram [wr_ptr] <= data_in;</pre>
end
//Read and Write Clock
always @ (posedge clk) begin: read
j if (rd && !empty)
data_out <= fifo_ram [rd_ptr];</pre>
else if (rd && wr)
data_out <= fifo_ram [rd_ptr];</pre>
end e
 //pointer block
always @(posedge clk) begin: pointer
j if (rst) begin
 wr_ptr <= 0;
 rd ptr <= 0;
end e
🗦 else begin
 wr_ptr <= ((wr && ! full) || (wr && rd)) ? wr_ptr+1 :
wr ptr;
```

#### 21EL034

```
wr_ptr;
rd_ptr <= ((rd && !empty) || (wr && rd)) ? rd_ptr+1:
rd ptr;
end
end
//counter
always @(posedge clk) begin: count
if (rst) fifo_cnt <= 0;
else begin
case ({wr, rd})
2'b00: fifo_cnt <= fifo_cnt;
2'b01: fifo_cnt <= (fifo_cnt==0) ? 0: fifo_cnt-1;
2'bl0: fifo_cnt <= (fifo_cnt==8) ? 8: fifo_cnt+1;
2'bll : fifo_cnt <= fifo_cnt;
default: fifo_cnt <= fifo_cnt;
endcase
end
end
endmodule
```


## **TESTBENCH:-**

```
module sync_fifo_tb();
  reg clk, rst, wr, rd;
 reg[7:0] data_in;
 reg[7:0] tempdata;
 wire [7:0] data_out;
 wire [3:0] fifo_cnt;
 sync_fifo fifo( .clk(clk), .rst(rst), .data_in(data_in), .data_out(data_out),
           .wr(wr), .rd(rd), .empty(empty),
           .full(full), .fifo_cnt(fifo_cnt));
initial
) begin
     clk = 0;
     rst = 1;
          rd = 0;
          wr = 0;
          tempdata = 0;
          data in = 0;
          #15 rst = 0;
          push (1);
          fork
             push (2);
             pop(tempdata);
         join
          push (10);
          push (20);
          push (30);
          push (40);
          push (50);
          push (60);
          push (70);
```

```
push (70);
          push (80);
          push (90);
          push (100);
          push (110);
          push (120);
          push (130);
          pop(tempdata);
          push (tempdata);
          pop(tempdata);
          pop(tempdata);
          pop(tempdata);
          pop(tempdata);
            push (140);
          pop(tempdata);
          push(tempdata);//
          pop(tempdata);
          push (5);
          pop(tempdata);
end)
3 always
#5 clk = ~clk;
```

```
always
   #5 clk = ~clk;
task push;
input[7:0] data;
   if(full)
           $display("---Cannot push: FIFO Full---");
        else
       begin
          $display("Pushed ",data);
          data_in = data;
          wr= 1;
               @(posedge clk);
               #1 wr = 0;
        end
endtask
task pop;
output [7:0] data;
   if( empty )
           $display("---Cannot Pop: FIFO Empty---");
   else
       begin
    rd = 1;
         @(posedge clk);
         #1 rd = 0;
         data = data_out;
          $display("-----Poped ", data);
⇒
endtask
         end
```

## RTL SCHEMATIC:-

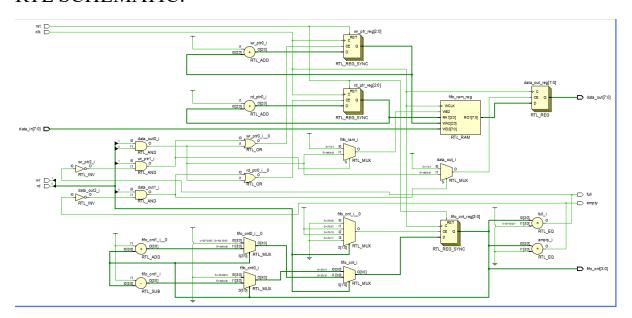

## SYNTHESIS REPORT:-

eport	t BlackBoxe	es:							
-+			+						
Bla	ackBox name	Instan	ces						
		+	+						
-	t Cell Usaç +								
, <b></b> .		Count							
	+								
1	BUFG								
2	LUT2								
3	LUT3	2							
4	LUT4	4							
5	LUT5	4							
6	LUT6	4							
17	RAM32M	2							
8	FDRE	18							
9	IBUF	12							
110	OBUF	14							
	+	+							
-	t Instance								
	+  Instance								
	+								
	top								
. –	-		-++						

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.239 W

Design Power Budget: Not Specified


Power Budget Margin: N/A

Junction Temperature: 31.1°C

Thermal Margin: 53.9°C (28.4 W)
Effective \$JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low

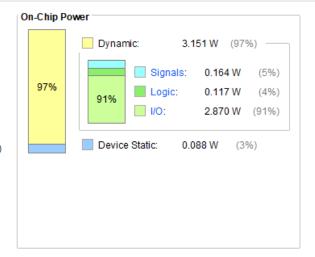Launch Power Constraint Advisor to find and fix



# Q20. PRIORITY ENCODER


## **VERILOG CODE:-**

```
module pri_en(d,y,en);
input [7:0] d;
input en;
output [2:0] y;
reg [2:0] y;
always @(d or en )
begin
if(en)
begin
casex(d)
8'b00000001:y=3'b000;
8'b0000001x:y=3'b001;
8'b000001xx:y=3'b010;
8'b00001xxx:y=3'b011;
8'b0001xxxx:y=3'b100;
8'b001xxxxx:y=3'b101;
8'b01xxxxxx:y=3'b110;
8'blxxxxxxx:y=3'bll1;
endcase
end
else
begin
y=3'bxxx;
end
end
endmodule
```

## **TEST BENCH:-**

```
module pri_en_tb();
reg [7:0] d;
reg en;
wire [2:0] y;
pri_en dut(d,y,en);
initial
begin
en=1'b1;
d=8'b00000001; #10;
d=8'b00000011; #10;
d=8'b00000101; #10;
d=8'b00001001; #10;
d=8'b00010001; #10;
d=8'b00110001; #10;
d=8'b01110001; #10;
d=8'b11001001; #10;
#10 d=8'b10111001;
#10 d=8'b00101010;
#10 d=8'b00000001;
#10 d=8'b10100010;
end
initial
$monitor("Input %8b | Output %3b | Enable %b ",d,y,en);
initial #100 $finish;
endmodule
```

## RTL SCHEMATIC:-

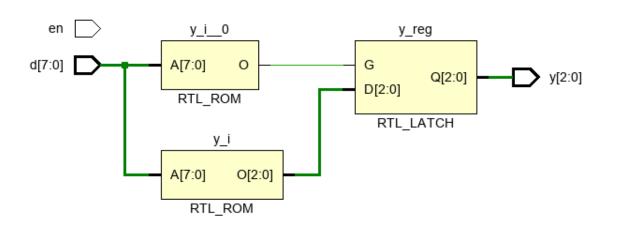

## SYNTHESIS REPORT:-

Start Writing Synthesis Report Report BlackBoxes: | |BlackBox name |Instances | Report Cell Usage: |Cell |Count | 11 |LUT4 | 2| 1| 12 |LUT5 | 13 |LUT6 | |LD | 3| |IBUF | 8| |OBUF | 3| 15 Report Instance Areas: |Instance |Module |Cells | Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16 . Memory (MB): peak = 1018.668 ; gain = 0.000

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.158 W

Design Power Budget: Not Specified


Power Budget Margin: N/A

Junction Temperature: 25.3°C

Thermal Margin: 59.7°C (31.5 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
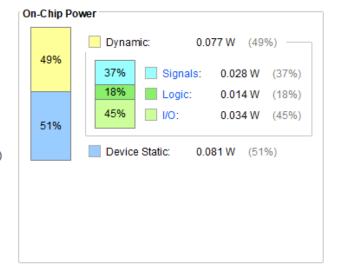
<u>Launch Power Constraint Advisor</u> to find and fix



## Q21. SEVEN SEGMENT DISPLAY USING ROM


#### **VERILOG CODE:-**

```
module ROM sevenSegment
  parameter addr_width = 16,
  addr bits = 4,
  data_width = 7
   )
   (
  input wire [addr bits-1:0] addr,
  output reg [data_width-1:0] data
) always @*
begin
case (addr)
  4'b00000 : data = 7'b10000000;
  4'b0001 : data = 7'b1111001;
  4'b0010 : data = 7'b0100100;
   4'b0011 : data = 7'b0110000;
  4'b0100 : data = 7'b0011001;
  4'b0101 : data = 7'b0010010;
  4'b0110 : data = 7'b00000010;
  4'b0111 : data = 7'b11111000;
  4'b1000 : data = 7'b00000000;
  4'b1001 : data = 7'b0010000;
  4'b1010 : data = 7'b0001000;
     4'b1011 : data = 7'b00000011;
     4'b1100 : data = 7'b1000110;
   4'b1101 : data = 7'b0100001;
  4'b1110 : data = 7'b0000110;
  default : data = 7'b0001110;
endcase
end)
) endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module ROM_sevenSegment_Test
   ();
   reg [3:0] SW;
  wire [6:0] HEX0;
  wire [6:0] LEDR;
 integer i;
  wire [6:0] data;
  ROM_sevenSegment seven_segment_ROM(.addr(SW), .data(data));
j initial begin
for(i=0;i<16;i=i+1)</pre>
begin
  SW=i;
  #10;
end end
end end
assign HEX0 = data;
  assign LEDR = data;
endmodule
```

## RTL SCHEMATIC:-

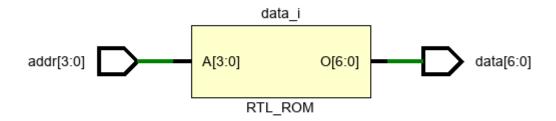

## SYNTHESIS REPORT:-

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 2.649 W


Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 30.0°C

Thermal Margin: 55.0°C (29.0 W)
Effective JA: 1.9°C/W

Power supplied to off-chip devices: 0 W
Confidence level: Low
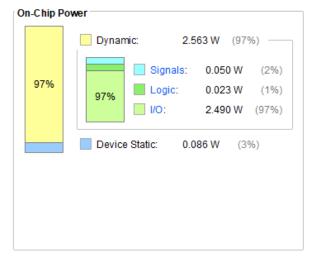
<u>Launch Power Constraint Advisor</u> to find and fix invalid switching activity



## Q22. SERIAL ADDER

## **VERILOG CODE:-**

```
`timescale lns / lps


    module serial_adder

      ( input clk, reset,
          input a,b,cin,
          output reg s, cout
          );
  reg c,flag;
always@(posedge clk or posedge reset)
begin
      if(reset == 1) begin
          s = 0;
          cout = c;
          flag = 0;
    end else begin
         if(flag == 0)
          begin
              c = cin;
              flag = 1;
          end
          cout = 0;
          s = a ^ b ^ c;
          c = (a \& b) | (c \& b) | (a \& c);
      end
end
endmodule
```

## **TESTBENCH:-**

```
module serial_adder_tb();
    reg clk;
    reg reset;
    reg a;
    reg b;
    reg cin;
    wire s;
    wire cout;
    serial_adder uut ( .clk(clk), .reset(reset), .a(a), .b(b), .cin(cin), .s(s), .cout(cout));
       #5 clk = ~clk;
    initial begin
       clk = 1; reset = 0;
       a = 0; b = 0; cin = 0; reset = 1;
       reset = 0;
        a = 1; b = 1; cin = 1;
       a = 1; b = 0; cin = 0; #10;
       a = 1; b = 1; cin = 0; #10;
       a = 1; b = 1; cin = 0; #10;
       reset = 1;
        #10;
       reset = 0;
       a = 1; b = 1; cin = 1;
                               #10;
        a = 1; b = 0; cin = 0; #10;
        a = 0; b = 0; cin = 0; #10;
        a = 1; b = 0; cin = 0; #10;
        a = 1; b = 1; cin = 0; #10;
       reset = 1;
        #10;
    end
    initial $monitor(" A=8b | B=8b | Cin=8b | Sum=8b | Cout=8b | Clock =8b",a,b,cin,s,cout,clk);
endmodule
```

## RTL SCHEMATIC:-

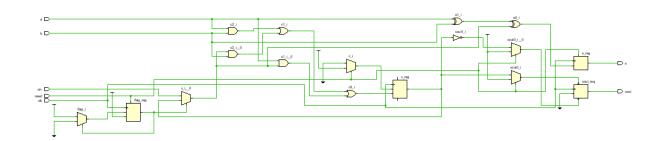

## SYNTHESIS REPORT:-

Start Writing Synthesis Report Report BlackBoxes: | |BlackBox name |Instances | +-+----Report Cell Usage: |Cell |Count | |BUFG | |LUT2 | 13 |LUT5 | |LUT6 | 15 | FDCE | |FDPE | 16 17 18 |LDC | |IBUF | 19 |10 |OBUF | 21 Report Instance Areas: |Instance |Module |Cells | |1 |top | | 18| Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:28 . Memory (MB): peak = 1014.773 ; gain = 0.000

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.618 W


Design Power Budget: Not Specified

Power Budget Margin: N/A
Junction Temperature: 26.2°C

Thermal Margin: 58.8°C (31.0 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

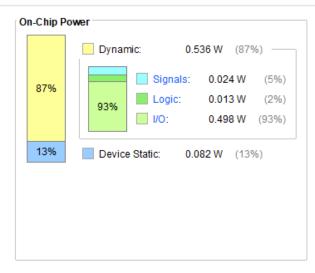Launch Power Constraint Advisor to find and fix




# Q23. FIXED PRIORITY ARBITER VERILOG CODE:-

```
module fixedpriority arbiter(output reg [3:0] GNT,
            input [3:0] REQ,
            input clk, reset
 );
 always @(posedge clk or negedge reset)
  // PRIORITY 3>1>0>2
     begin
     if(!reset)
    GNT<= 4'b0000;
    else if(REQ[3])
     GNT<= 4'b1000;
    else if(REQ[1])
     GNT<= 4'b0010;
    else if(REQ[0])
     GNT<= 4'b0001;
    else if(REQ[2])
      GNT<= 4'b0100;
      else
     GNT<= 4'b00000;
     end
endmodule
```

## **TESTBENCH:-**

```
`timescale lns / lps
module fixedpriority_arbiter_tb();
  wire [3:0] GNT;
  reg [3:0] REQ;
  reg clk, reset ;
  fixedpoint_arbiter dut(.GNT(GNT),.REQ(REQ),.clk(clk),.reset(reset));
initial (
clk=0;
  always #4 clk <= ~clk ;
j initial
begin
 reset =0;
  #4 reset =1;
] repeat (20)
begin
#5 REQ<=$random();</pre>
end
 #100 $finish();
end
j initial begin
  $monitor("REQ=%b,GNT=%b,reset=%b",REQ,GNT,reset);
endmodule
```

## RTL SCHEMATIC:-

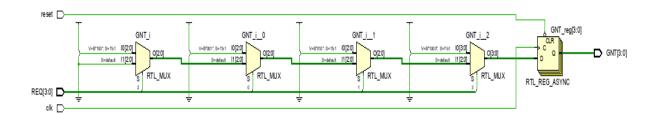

## SYNTHESIS REPORT:-

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.861 W

Design Power Budget: Not Specified


Power Budget Margin: N/A
Junction Temperature: 26.6°C

Thermal Margin: 58.4°C (30.8 W)

Effective 9JA: 1.9°C/W
Power supplied to off-chip devices: 0 W

Confidence level: Low

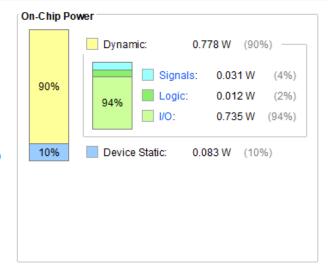Launch Power Constraint Advisor to find and fix



# Q24. ROUND ROBIN ARBITER VERILOG CODE:-

```
`timescale lns / lps
module roundrobin arbiter(
  input clk, rst_n,
  input [3:0] REQ,
  output reg [3:0] GNT
     );
      reg[2:0] pr state;
     reg[2:0] nxt_state;
     parameter [2:0] Sideal = 3'b000;
     parameter [2:0] S0 = 3'b001;
     parameter [2:0] S1 = 3'b010;
     parameter [2:0] S2 = 3'b011;
     parameter [2:0] S3 = 3'b100;
9
     always @(posedge clk or negedge rst_n)
9
     begin
9
     if(!rst_n)
      pr_state <= Sideal;</pre>
      else
Ė
      pr_state <=nxt_state;
      end
Ė
9
     always@(*)
9
    begin
9
           case (pr_state)
9
              Sideal:
9
                      begin
9
                           if(REQ[0])
                              nxt_state = S0;
9
                           else if (REQ[1])
                               nxt_state = S1;
9
                          else if (REQ[2])
                             nxt state = S2;
```

```
always@(*)
begin
      case(pr_state)
        Sideal:
                 begin
                     if(REQ[0])
                         nxt_state = S0;
                     else if (REQ[1])
                         nxt state = S1;
                     else if (REQ[2])
                        nxt_state = S2;
                     else if (REQ[3])
                        nxt_state = S3;
                      else
                         nxt state =Sideal;
                 end
           S0:
                 begin
                     if (REQ[1])
                        nxt_state = S1;
                     else if (REQ[2])
                        nxt_state = S2;
                     else if (REQ[3])
                         nxt_state = S3;
                     else if(REQ[0])
                         nxt_state =S0;
                     else
                         nxt_state =Sideal;
                 end
           S1:
                 begin
                     if (REQ[2])
                        nxt_state = S2;
                     else if (REQ[3])
```


```
S1:
     begin
          if (REQ[2])
             nxt_state = S2;
          else if (REQ[3])
              nxt state = S3;
          else if(REQ[0])
              nxt_state =S0;
           else if (REQ[1])
            nxt state = S1;
             else
             nxt_state =Sideal;
     end
S2:
     begin
        if (REQ[3])
              nxt_state = S3;
         else if(REQ[0])
              nxt_state =S0;
           else if (REQ[1])
            nxt_state = S1;
             else if (REQ[2])
             nxt_state = S2;
             else
             nxt_state =Sideal;
      end
 S3:
     begin
             if(REQ[0])
              nxt_state =S0;
            else if (REQ[1])
             nxt_state = S1;
             else if (REQ[2])
             nxt_state = S2;
             else if (REQ[3])
```

```
nxt_state = S2;
Э
                           else if (REQ[3])
                              nxt_state = S3;
                            else
È
                               nxt state =Sideal;
-)
                      end
É
         endcase
Ė
  end
9
      always @(*)
      begin
Э
          case (pr state)
          S0: GNT=4'b0001;
          S1: GNT=4'b0010;
          S2: GNT=4'b0011;
          S3: GNT=4'b0100;
          default: GNT=4'b0000;
          endcase
end
endmodule
```

### **TESTBENCH:-**

```
`timescale lns / lps
module roundrobin_arbiter_tb();
   reg clk;
    reg rst_n;
    reg [3:0] REQ;
    wire [3:0] GNT;
    roundrobin_arbiter DUT(.clk(clk), .rst_n(rst_n), .REQ(REQ), .GNT(GNT));
    always #5 clk = ~clk;
  initial begin
     clk = 0;
      rst_n = 1;
     REQ = 4'b0;
      #5 rst_n = 1;
      @(negedge clk) REQ = 4'bl000;
      @(negedge clk) REQ = 4'b1010;
      @(negedge clk) REQ = 4'b0010;
      @(negedge clk) REQ = 4'b0110;
      @(negedge clk) REQ = 4'bl110;
      @(negedge clk) REQ = 4'bllll;
      @(negedge clk) REQ = 4'b0100;
      @(negedge clk) REQ = 4'b0010;
      #5 rst n = 0;
      #100 $finish;
    end
   endmodule
```

## RTL SCHEMATIC:-

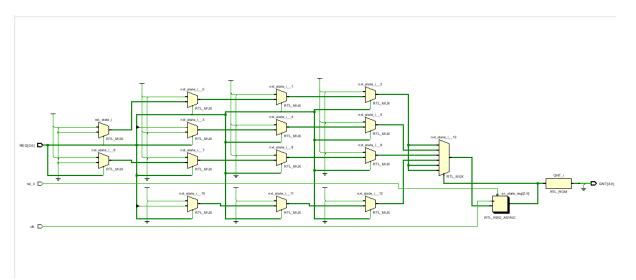

## **SYNTHESIS REPORT:-**

Start Writing Synthesis Report

#### Report BlackBoxes:

| |BlackBox name |Instances | +-+-----+

#### Report Cell Usage:

+	-+	-++
1	Cell	Count
+	-+	-++
11	BUFG	1
12	LUT1	1
13	LUT2	2
4	LUT3	2
15	LUT5	1
16	LUT6	4
17	MUXF7	2
18	FDCE	3
19	IBUF	6
10	OBUF	4
+	-+	-++

#### Report Instance Areas:

	Instance	Module	Cell	.s
1	top	l	 	26

Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:25 . Memory (MB): peak = 1017.727 ; gain = 0.000

## POWER REPORT:-

#### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 1.408 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 27.7°C

Thermal Margin: 57.3°C (30.3 W)

Effective \$JA: 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

Launch Power Constraint Advisor to find and fix

